



Shri Shankaracharya Institute of Professional Management & Technology, Raipur

February-2022- Class Test-2

Date: 07/02/2022

Student Name: V OM SAI NAGESHWAR SHARMA

Roll No.:

3	0	3	3	0	2	2	2	0	0	2	0
---	---	---	---	---	---	---	---	---	---	---	---

Enrollment No.:

B	J	4	5	9	9
---	---	---	---	---	---

Course: B.Tech **Semester:** 3rd

Branch: Computer Science And Engineering

Subject Name: Digital Electronics

Subject Code:

B	0	2	2	3	1	4
---	---	---	---	---	---	---

(0	2	2)
---	---	---	---	---

Mobile No.: 8602727389

Email id: om.sharma@ssipmt.com


Signature: 

PART - I

 
Q1

Ans \Rightarrow Race around condition:- In level triggering triggered J.K. flip-flop when ($J=K=1$) both the inputs are 1, and without changing the input ~~are 1, and without~~ if output gets changed (toggled) then this is called race Around condition.

In J.K. flip-flop, The output is feedback to the input, and therefore change in the output results change in the ~~input~~ input, if the inputs $J=K=1$. Assume $Q=0$. when a clock pulse with a width t_p as shown in below is applied, output will change from 0 to 1 after the time interval Δt .



 Input and Output waveform for master-slave flip-flop: The output state of the master flip-flop is determined by the J and K ~~is~~ input at the positive clock pulse. The output state of the master is then transferred as an input to the slave flip-flop. The ~~set~~ slave flip-flop uses this input at the negative clock pulse to determine output state.



Truth table for Master output:

Clock Pulse	J	K	Master Output
1	1	0	1 (Set)
3	0	1	0 (reset)
5	0	0	0 (NC)

Truth table for slave output :

Clock Pulse	Master Output	Slave output
2	1 (set)	1 (set)
4	0 (reset)	0 (reset)
6	0 (NC)	0 (NC)


 



fig: Input and output waveforms for clocked JK flip-flop.

 The race around condition can be eliminated when $t_p < \Delta t$.



The value of t_p can be reduced by using a pulse generator to produce less pulse width waveform, but it is difficult to get such type of circuit.

 
The value of Δt can be increased by using the lumped delay lines in series with the feedback connection, which is worthless.



 Q3

Ans \Rightarrow

Two Input TTL NAND gate with totem-Pole output:



Truth Table for 2-input NAND gate:

Input		Transistor		Output
A	B	Q_2	Q_4	Y
0	0	cutoff	cutoff	1
0	1	cutoff	cutoff	1
1	0	cutoff	cutoff	1
1	1	Saturation	Saturation	0

Circuit Operation:

- 1.) The output is taken from the collector of transistor Q_4 . Each emitter of Q_1 acts like a diode. Therefore, transistor Q_1 and the $4\text{K}\Omega$ resistor act like a 2-input AND gate and the rest of the circuit inverts the signal. Hence, the overall circuit acts like a 2-input NAND gate.
- 2.) When either or all inputs (A and B) are at 0V (logic 0), the corresponding emitter-base junction of Q_1 becomes forward-biased. The value of R_B is selected so as to ensure that Q_1 is turned ON. However, the value of current I_B flowing through the base of Q_4 are cutoff so that the output voltage is at V_{CC} (logic 1).

3. If all the inputs are high (logic 1), the emitter-base junction of Q_1 is reverse-biased so that it has no base current. Hence, Q_1 is off. However, its collector-base junction is forward-biased supplying base current I_{B1} to Q_2 . The current I_{B2} will be sufficiently large to saturate Q_2 . As a result, transistor Q_2 is turned ON and the drop across R_2 is sufficient to forward bias the base-emitter junction of Q_4 , therefore turning Q_4 ON. Hence, the output at its collector is low (logic 0). The function of diode D is to prevent both Q_2 and Q_4 from being ON simultaneously.

4.) In the absence of diode D, the transistor Q_3 will conduct slightly when the output is LOW. In order to prevent this, the diode is connected between the emitter of Q_3 and the collector of Q_4 . The voltage drop across the diode keeps the base-emitter junction of Q_3 reverse-biased. In this way, transistor Q_4 only conducts when the output is LOW, which confirms the conditions for NAND operation.

5.) Transi Q_3 and Q_4 form a Totem-pole transistors are used because they produce a low output impedance. Either Q_1 , acts as an emitter follower (High output), or Q is saturated (low output).

Part - II

Q.2

Ans \Rightarrow

CMOS \rightarrow The term CMOS stands for complementary metal oxide semiconductor. This is the one of the most popular technology in the computer chip used to form integrated circuits in numerous and varied.

CMOS NAND Gate:

A 2-input CMOS NAND gate consists of two series NMOS transistors between Y and Ground and two parallel PMOS transistors between Y and VDD .


\rightarrow If either input A or B is logic 0, atleast one of the NMOS transistors will be off, breaking the path from Y to ground.

But atleast one of the PMOS transistor is ON, creating a path from V to V_{DD} .

Two input
Truth Table:

V_A	V_B	V_{out}
Low	Low	High
Low	High	High
High	Low	High
High	High	Low

Circuit:

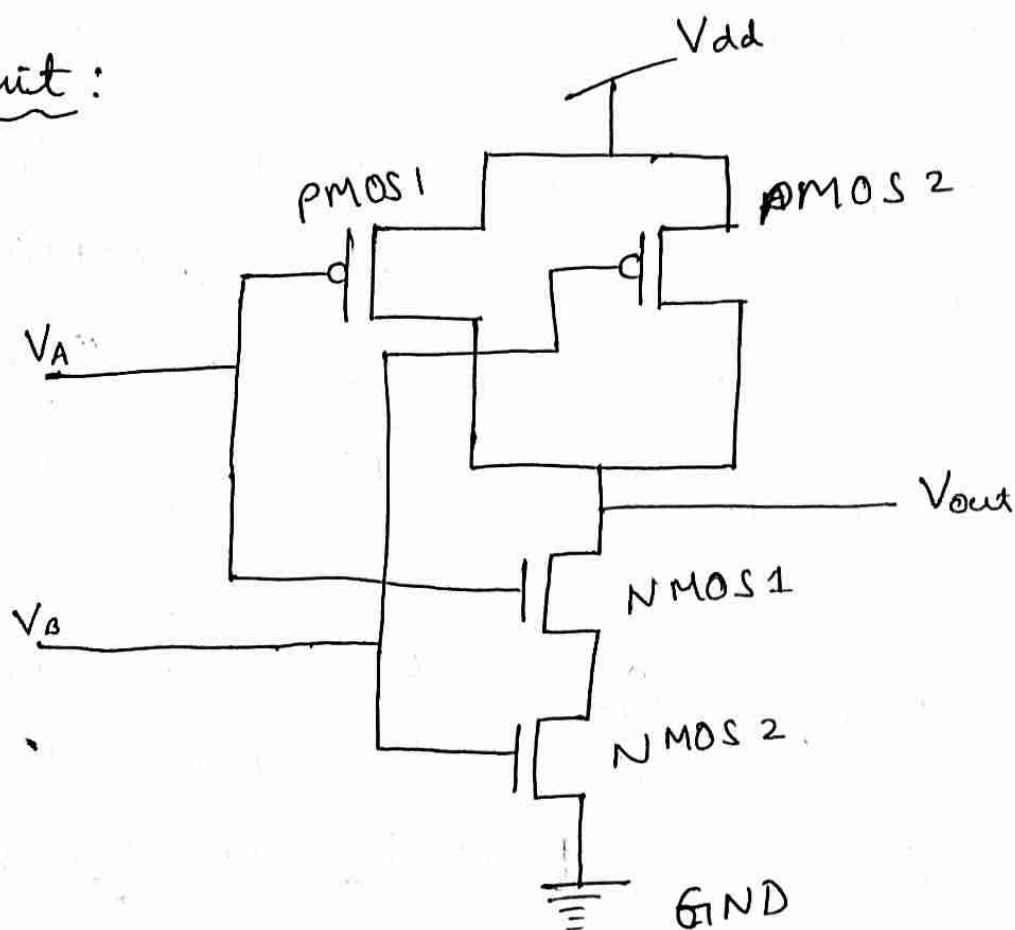

Case-1 $V_A - \text{Low} \ \& \ V_B = \text{Low}$

As V_A and V_B both are low, both the pMOS will be ON and both the nMOS will be OFF. So the output V_{out} will get two paths through two ON pMOS to get connected with V_{dd} . The output will be charged to the V_{dd} level.

The output line will not get any path to the GND as both the nMOS are off. So, there is no path through which the output line can discharge. The output line will maintain the voltage level at V_{dd} so high.

Case - 2: V_A - low & V_B - high

V_A - low: pMOS1 - ON; nMOS1 - OFF

V_B = high: pMOS2 - OFF; nMOS2 - ON

pMOS1 and pMOS2 are in parallel.

Through pMOS is off, still the output line will get a path through pMOS1 to get connected with Vdd. nMOS1 and nMOS2 are in series. As nMOS1 is OFF, so V_{out} will not be able to find a path to GND to get discharged. This is turn results the V_{out} to be maintained at the level of Vdd. so High.

Case - 3: V_A - High & V_B - Low

V_A - High: pMOS1 - off; nMOS1 - ON

V_B - LOW: pMOS2 - ON; nMOS2 - OFF

The explanation is similar as cas2
 V_{out} level will be High.

Case - 4: V_A - High & V_B - High

V_A - High: pMOS1 - OFF; nMOS1 - ON

V_B - High: pMOS2 - OFF; nMOS2 - ON

Answer = 3

when counter is clocked such that each flip-flop in the counter is triggered at the same time. the counter is called as Synchronous counter.

Below figure shows a two stage synchronous counter

 


fig 2-bit synchronous binary counter

Here clock signal is connected in parallel to clock inputs of both the flip-flops.

But QA output of first stage is used to drive the J and K inputs of the second stage.

Operation of the circuit

Initially - we assume that the
 $QA = QB = 0$.

When positive edge of first clock pulse is applied, flip-flop A will toggle because $J_A = K_A = 1$, whereas flip-flop B output will remain zero because $J_B = K_B = 0$.

CP	QB	QA
0	0	0
1	0	1
2	1	0
3	1	1

(b) State Sequence.

fig. Timing diagram (a) and state sequence (b) for 2-bit synchronous counter.

