

Electric Circuit :- Circuit may be define is the combination of active, and passive elements are called circuit.

→ Linear Elements :- It is the circuit whose parameter remain constant with change in applied voltage and current.
Ex. - Resistance, inductance or capacitance.

→ Non-Linear Elements :- It is the circuit whose parameter change with voltage or current.
Ex. Semi-conductor resistor.

Note : The linear circuit obey the Ohm's law i.e. current is directly proportional with applied voltage.
But non-linear circuit, Ohm's law is not satisfied.

→ Unilateral circuit :- When the direction of current is changed, the characteristic or property of the circuit may be

Teacher's Signature.....

change. In this case unilateral circuit.
Ex: Diode, Transistor etc.

→ Bilateral circuit:- When the change in direction of current, the direction of characteristic or properties of the circuit may not change, it is called Bilateral circuit. Ex:- Mostly, element made of high conductivity material are Bilateral circ.

→ Active Element:- The active element are those element which delivered ~~the~~ energy. called Active element.
Ex: Battery, source of e.m.f.

→ Passive Element:- The passive element are those element which absorbed energy. called passive element.
Ex: Resistance, Inductance, capacitance etc.

Resistance :- The electrical resistance is the property of a material due to which it opposes the flow of electron through the material or it opposes the flow of electric current. The unit of resistance is ohm (Ω).

$$R = \frac{V}{I}$$

Power absorbed by the resistors is

$$P = VI = (IR) \cdot I = I^2 R \text{ watt.}$$

Energy lost in the form of heat is

$$W = \int_0^t P \cdot dt = Pt.$$

$$= I^2 R \cdot t$$

$$W = \frac{V^2}{R} \cdot t$$

Inductance :- The inductance is the property of material due to which it opposes any change of magnitude or direction of electric current passing through the conductor. The unit of inductance is Henry (H).

$$V_L = -L \frac{di}{dt}$$

In case of pure inductive

$$V + V_L = 0$$

$$V = -V_L = L \frac{di}{dt}$$

Power absorbed by the inductor

$$P = V i = L i \frac{di}{dt} \text{ Watt}$$

Energy absorbed by the inductor

$$W = \int_0^t P dt = \int_0^t L i \frac{di}{dt} dt$$

$$W = \frac{1}{2} L i^2$$

Capacitance :- The capacitance is a property of material due to which store the charges i.e. electric charges. The unit of capacitance is farad (F).

$$Q = CV, \quad C = \frac{Q}{V}$$

$$i = C \frac{dV}{dt} \quad \left[\because i = \frac{dQ}{dt} \right]$$

Power absorbed by the capacitor

$$P = V i = V \cdot C \frac{dV}{dt} \text{ Watt.}$$

Energy absorb by the capacitor is

$$W = \int_0^t P \cdot dt = \int_0^t V C \frac{dV}{dt} \cdot dt$$

$$W = \frac{1}{2} C V^2$$

| Circuit elemt | Voltage (volts) | Current (amps) | Power (watt) |
|---------------|-----------------------------|-----------------------------|------------------------|
| $R(\Omega)$ | $V = Ri$ | $i = \frac{V}{R}$ | $P = i^2 R$ |
| $L(H)$ | $V = L \frac{di}{dt}$ | $i = \frac{1}{L} \int V dt$ | $P = Li \frac{di}{dt}$ |
| $C(F)$ | $V = \frac{1}{C} \int i dt$ | $i = C \frac{dV}{dt}$ | $P = CV \frac{dV}{dt}$ |

Ques A 100Ω resistance is directly switched on across a $10V$ battery. What is the current through the resistor? How much the power losses? Also find the energy consumed in 5 sec.

Soln:- Given that $V = 10V$, $R = 100\Omega$

$$I = \frac{V}{R} = \frac{10}{100} = 0.1 A$$

$$\text{Power loss} = I^2 R = (0.1)^2 \times 100 = 1 \text{ watt.}$$

$$\text{Energy consumed} = I^2 R t = 1 \times 5 \text{ watt sec.}$$

$$= 5 \text{ Joules}$$

Ques: The strength of current in 1 H inductor changes at a rate of 1 A/sec . find the vtg across it and determine the magnitude of energy stored in the inductor after 2 sec .

Sol: $L = 1\text{ H}$, $\frac{di}{dt} = 1\text{ A/sec}$.

$$V = L \frac{di}{dt} = 1 \times 1 = 1\text{ V}$$

$$\text{Energy stored } W = \frac{1}{2} \cdot L i^2 = \frac{1}{2} \times 1 \times 2^2 \quad (i = 2\text{ sec})$$

$$W = 2\text{ Joules} \quad (i = 2\text{ A})$$

Ques: A capacitor has a capacitance of $5\text{ }\mu\text{F}$. calculate the stored energy in it if a d.c. vtg of 100 V is applied across it.

Sol: $V = 100\text{ V}$, $C = 5 \times 10^{-6}\text{ F}$

$$W = \frac{1}{2} C V^2 = \frac{1}{2} \times 5 \times 10^{-6} \times (100)^2$$

$$W = 2.5 \times 10^{-2}\text{ Joules}$$


Energy Sources :- There are many two type of energy sources.

① Direct source ② Alternating source.

And this two sources are further subclassified as dependent source and independent source.

① Direct Source :- Independent voltage and current source have been shown in fig.

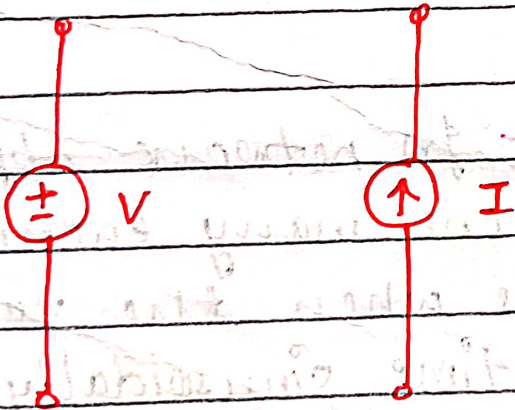
The strength of voltage or current is not changed by any variation in a connected network.




Independent-
voltage source

Independent
current source.

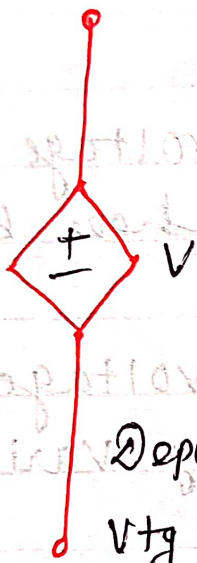When strength of voltage or current changes in the source for any change in the connected network they are called **Dependent source**. Dependent voltage or current sources are shown in fig.



Dependent
vty source

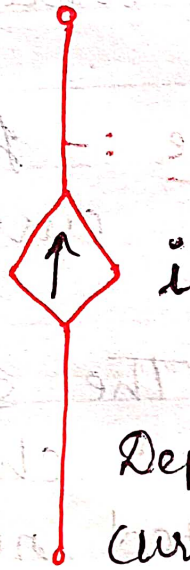

Dependent
current source.

② Alternating Sources:- In network application one may encounter other type of sources when the voltage or current vary with time sinusoidally, exponentially etc.

| Basis For Comparison | Electrical Device | Electronics Device |
|-----------------------------|---|---|
| Definition | It is defined as the device which uses the electrical energy for performing the work. | The device which controls the flow of electrons for performing the particular task is known as the electronics devices. |
| Material Used | Metals like copper and aluminum are used for the conduction of current. | Semiconductor material like silicon, germanium etc. |
| Operating Principle | Convert the electrical energy into other forms of energy. | Uses the electrical energy for performing the particular task. |
| Current | Alternating Current | Direct Current |
| Voltage | Works on high voltage. | Works on low voltage |
| Power consumption | More | Less |
| Manipulation | Do not manipulate the data | It manipulates the data. |
| Response Time | Fast | Slow |
| Required Space | More | Less |
| Safe | Less | More |
| Uses | For doing mechanical work. | For amplifying the weak signal or for coding and decoding the information. |
| Examples | Transformer, motor, generator etc. | Transistor, diode, microprocessor, flip-flop, amplifier, etc. |